

Date: 4-06-2021

Class: 10<sup>th</sup> Genesis

**Subject:** Science

Test code: SEP06(21041306)

## **Physics**

M. Marks: 20

1. An electric geyser has the ratings 2000W, 220 V marked on it. What should be the minimum rating, in whole number of a fuse wire, that may be required for safe use with this geyser? (1 marks)

- 2. Two metallic wires A and B are connected in parallel. Wire A has length I and radius r, wire B has a length 2I and radius 2r. Compute the ratio of the total resistance of parallel combination and the resistance of wire A. (1 marks)
- 3. Find the magnetic field intensity at the centre of coil of 50 turns, radius 0.5 m and carrying a current of 2A. (1 marks
- 4. The electric power consumed by a device may be calculated by using either of the two expressions
  - $P=I^2 R$  or  $P=\frac{V^2}{R}$ . The first expression indicates that it is directly proportional to R whereas the

second expression indicates inverse proportionality. How can the seemingly different dependence of P on R in these expression be explained? (2 marks)

5. In the Bohr model of the hydrogen atom, the Single electron circulates around the nucleus in a path of radius  $5.1\times10^{-11}$  m with a time period of  $0.14\times10^{-15}$  s. What is the magnetic field set – up at the centre of orbit?

(2 marks)

- 6. A current through a horizontal power line flows in east to west direction. What is the direction of magnetic field at a point directly below it and at a point directly above it? (2 marks)
- 7. A torch bulb is rated 5.0 V and 500 mA. Calculate its (i) power (ii) resistance and (iii) energy consumed when it is lighted for 4 hours. (2 marks)
- 8. A circular loop of larger radius will produce stronger magnetic field than a loop of smaller radius, if same current is flowing through both the loops. It is true or false? Explain. (2 marks)
- 9. Two resistors when connected in series give resultant value 9  $\Omega$  and when connected in parallel, the value becomes 2  $\Omega$ . Find the value of each resistor. (3 marks)
- 10. What is electric power? Derive expression for the same. Give its S.I. unit. (3 marks)
- 11. A household uses the following electric appliances:

(3 marks)

- (i) Refrigerator of rating 400 W for ten hours each day.
- (ii) Two electric fans of rating 80 W each for twelve hours each day.
- (iii) Six electric tubes of rating 18 W each for 6 hours each day.

Calculate the electricity bill of the household for the month of June if the cost per unit of electric energy is Rs. 3.00.

